

GROUP 14

4-bit Carry Look-Ahead Adder v/s Ripple Carry Adder

PRESENTED BY 15 DILJITH OR 47 PETER AJITH CHERIAN

INTRODUCTION

4 bit carry look-ahead adder is a type of adder used in digital circuits to add binary numbers **fast and efficiently** .

Unlike a ripple carry adder, it speeds up the process by **calculating carries in advance**.

This is a fundamental concept in **designing high speed arithmetic logic units** (ALUs) in modern processors.


OBJECTIVES

- Design a **4-bit Carry Look-Ahead Adder (CLA)** using Verilog.
- Compare its performance with a **Ripple Carry Adder (RCA)**.
- Implement both designs on an FPGA.
- Measure key performance metrics such as **delay** and **power consumption**.

SCOPE

- **Design** : Implement CLA and RCA adders using Verilog HDL.
- **Test** : Simulate both designs with Icarus Verilog.
- **Implement** : Deploy on an FPGA for real-world performance testing.
- **Analyze** : Compare propagation delay, area, and power consumption.
- Suitable for high-performance systems like CPUs, DSPs, and microcontrollers, where fast arithmetic operations are essential.

BLOCK DIAGRAM

 

 


FIGURE 4.9
Four-bit adder

four-bit binary ripple carry adder.

Example.

Consider the two binary numbers A = 1011 and B = 0011.

Their sum S = 1110 is formed with the four-bit adder as :

Subscript i:	3	2	1	0	
Input carry	0	1	1	0	C_i
Augend	1	0	1	1	A_i
Addend	0	0	1	1	B_i
Sum	1	1	1	0	S_i
Output carry	0	0	1	1	C_{i+1}

Four-bit Full Adder with Carry Lookahead

Carry look ahead logic.

C_0 = input carry

$C_1 = G_0 + P_0C_0$

$C_2 = G_1 + P_1C_1 = G_1 + P_1(G_0 + P_0C_0) = G_1 + P_1G_0 + P_1P_0C_0$

$C_3 = G_2 + P_2C_2 = G_2 + P_2G_1 + P_2P_1G_0 + P_2P_1P_0C_0$

 


FIGURE 4.11
Logic diagram of carry lookahead generator

 


FIGURE 4.12
Four-bit adder with carry lookahead

DESIGN

1. 4-bit Ripple Carry Adder (RCA)

This design uses a series of 1-bit full adders.

1-bit Full Adder Code

```
1 | module full_adder (  
2 |     input A, B, Cin,  
3 |     output Sum, Cout  
4 | );  
5 |     assign Sum = A ^ B ^ Cin;           // Sum = A XOR B XOR Cin  
6 |     assign Cout = (A & B) | (Cin & (A ^ B)); // Cout = AB + Cin(A XOR B)  
7 | endmodule
```

4-bit Ripple Carry Adder Code

```
1 module ripple_carry_adder_4bit (  
2     input [3:0] A, B,  
3     input Cin,  
4     output [3:0] Sum,  
5     output Cout  
6 );  
7     wire C1, C2, C3; // Internal carry wires  
8  
9     // Instantiate 1-bit full adders  
10    full_adder FA0(A[0], B[0], Cin, Sum[0], C1);  
11    full_adder FA1(A[1], B[1], C1, Sum[1], C2);  
12    full_adder FA2(A[2], B[2], C2, Sum[2], C3);  
13    full_adder FA3(A[3], B[3], C3, Sum[3], Cout);  
14 endmodule
```


2. 4-bit Carry Look-Ahead Adder (CLA)

```
1 module carry_lookahead_adder_4bit (  
2     input [3:0] A, B,  
3     input Cin,  
4     output [3:0] Sum,  
5     output Cout  
6 );  
7     wire [3:0] G, P;    // Generate and Propagate signals  
8     wire C1, C2, C3;    // Internal carry signals  
9  
10    // Generate and Propagate Logic  
11    assign G = A & B;    // Generate:  $G_i = A_i \& B_i$   
12    assign P = A | B;    // Propagate:  $P_i = A_i | B_i$   
13  
14    // Carry Look-Ahead Logic  
15    assign C1 = G[0] | (P[0] & Cin); //  $C1 = G_0 + P_0 * Cin$   
16    assign C2 = G[1] | (P[1] & C1);  //  $C2 = G_1 + P_1 * C1$   
17    assign C3 = G[2] | (P[2] & C2);  //  $C3 = G_2 + P_2 * C2$   
18    assign Cout = G[3] | (P[3] & C3); //  $Cout = G_3 + P_3 * C3$   
19  
20    // Sum Calculation  
21    assign Sum[0] = A[0] ^ B[0] ^ Cin; //  $Sum_0 = A_0 \text{ XOR } B_0 \text{ XOR } Cin$   
22    assign Sum[1] = A[1] ^ B[1] ^ C1;  //  $Sum_1 = A_1 \text{ XOR } B_1 \text{ XOR } C1$   
23    assign Sum[2] = A[2] ^ B[2] ^ C2;  //  $Sum_2 = A_2 \text{ XOR } B_2 \text{ XOR } C2$   
24    assign Sum[3] = A[3] ^ B[3] ^ C3;  //  $Sum_3 = A_3 \text{ XOR } B_3 \text{ XOR } C3$   
25 endmodule
```

3. Testbench for Both Adders

```
1 module testbench();
2     reg [3:0] A, B;
3     reg Cin;
4     wire [3:0] Sum_RCA, Sum_CLA;
5     wire Cout_RCA, Cout_CLA;
6     // Instantiate the RCA
7     ripple_carry_adder_4bit RCA (
8         .A(A),
9         .B(B),
10        .Cin(Cin),
11        .Sum(Sum_RCA),
12        .Cout(Cout_RCA)
13    );
14    // Instantiate the CLA
15    carry_lookahead_adder_4bit CLA (
16        .A(A),
17        .B(B),
18        .Cin(Cin),
19        .Sum(Sum_CLA),
20        .Cout(Cout_CLA)
21    );
22    initial begin
23        // Test cases
24        A = 4'b0000; B = 4'b0000; Cin = 0; // Test Case 1
25        #10; // Wait for 10 time units
26
27        A = 4'b0011; B = 4'b0001; Cin = 0; // Test Case 2
28        #10;
29
30        A = 4'b0110; B = 4'b0101; Cin = 1; // Test Case 3
31        #10;
32
33        A = 4'b1111; B = 4'b1111; Cin = 1; // Test Case 4
34        #10;
35        // End simulation
36        $finish;
37    end
38
39    initial begin
40        // Monitor outputs
41        $monitor("A = %b, B = %b, Cin = %b | Sum_RCA = %b, Cout_RCA = %b | Sum_CLA = %b, Cout_CLA = %b",
42            A, B, Cin, Sum_RCA, Cout_RCA, Sum_CLA, Cout_CLA);
43    end
44 endmodule
```

SOFTWARE/HARDWARE REQUIREMENTS

Software:

- Icarus Verilog: Used for simulation and verification of Verilog designs.
 - Verilog files for CLA and RCA.
 - Testbenches to verify functionality.
- GTKWave: To view simulation waveforms and analyze timing.


Hardware:

- FPGA development board (Xilinx FPGA).
- Synthesis Tools: Xilinx Vivado for FPGA deployment.


BILL OF MATERIALS (BOM)

- **FPGA Development Board (Xilinx):** Used for hardware implementation.
- **Icarus Verilog:** Open-source Verilog simulator.
- **HDL Design Tools (Vivado):** For synthesis and deployment.
- **Power Supply & Peripheral Devices:** Required for the FPGA board.

SIMULATION O/P

 

FPGA IMPLEMENTATION

 

CONCLUSION

This project effectively implements a 4-bit Carry Look-Ahead Adder using Verilog. The 4-bit Carry Look-Ahead Adder offers faster addition by reducing the delay caused by ripple carry propagation.

Tests and adjustments were carried out to verify the correct operation of the 4-bit Carry Look-Ahead Adder, and the results produced by the code have been demonstrated.

The 4 Bit Carry Look-Ahead Adder significantly improves addition speed by minimizing carry propagation delays, making it ideal for high-performance computing tasks.

REFERENCES

- Digital Design by Morris Mano
- <https://www.gatevidyalay.com/carry-look-ahead-adder/> (Block diagram)
- <https://stackoverflow.com/questions/68964488/verilog-test-bench-for-4-bit-adder-with-carry-lookahead> (Test Bench)
- <https://nandland.com/carry-lookahead-adder/> (ideas)
- https://github.com/roboticvedant/CLA_4bit_adder